

# Random Walks and Electric Networks

Rajeev Atla<sup>1</sup>    Quentin Dubroff<sup>2</sup>

<sup>1</sup>Mentee

<sup>2</sup>Mentor

Fall 2021 DRP Presentation

# Table of Contents

- 1 Introduction
- 2 References
- 3 Definitions
- 4 Using Random Walks
- 5 Polya's Theorem

# References

- Doyle and Snell - *Random walks and electric networks* [1]

# Introduction: Definitions

- **Random walk** - a random process that consists of random steps on some mathematical space e.g.  $\mathbb{Z}$

# Introduction: Definitions


- **Random walk** - a random process that consists of random steps on some mathematical space e.g.  $\mathbb{Z}$
- **Electric network** - an interconnection of electric components
  - We only care about resistors

# A Random Walk

- Consider a random walk over the set  $[0, N] \cap \mathbb{Z}$

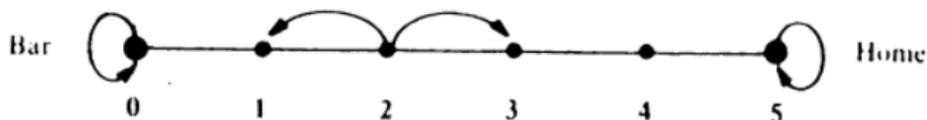
# A Random Walk

- Consider a random walk over the set  $[0, N] \cap \mathbb{Z}$
- Suppose a drunk man walks along a street with  $N$  blocks, arranged as follows


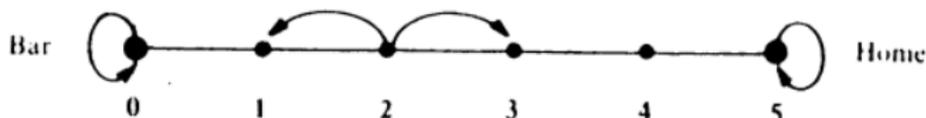
# A Random Walk

- Consider a random walk over the set  $[0, N] \cap \mathbb{Z}$
- Suppose a drunk man walks along a street with  $N$  blocks, arranged as follows



- **Escape probability** - the probability of never going to the bar (origin) i.e. going home before going to the bar

# Recurrence Relation

- Let  $p(x)$  be the solution


# Recurrence Relation

- Let  $p(x)$  be the solution
- 1  $p(0) = 0$
- 2  $p(N) = 1$
- 3  $p(x) = \frac{1}{2}p(x - 1) + \frac{1}{2}p(x - 1)$  (Law of Total Probability)


# Recurrence Relation

- Let  $p(x)$  be the solution
- 1  $p(0) = 0$
- 2  $p(N) = 1$
- 3  $p(x) = \frac{1}{2}p(x-1) + \frac{1}{2}p(x-1)$  (Law of Total Probability)
- Uniqueness theorem can be proved

# Similar Problem ?!

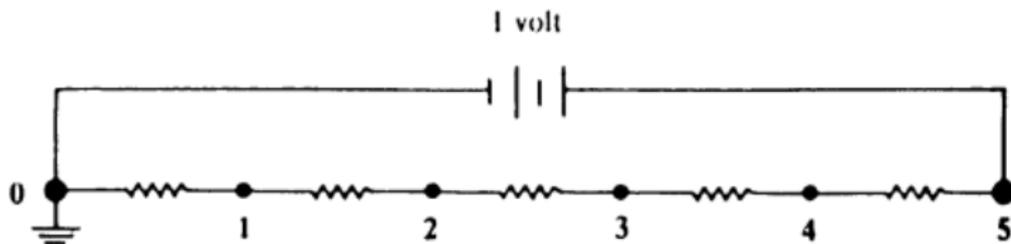


# Similar Problem ?!

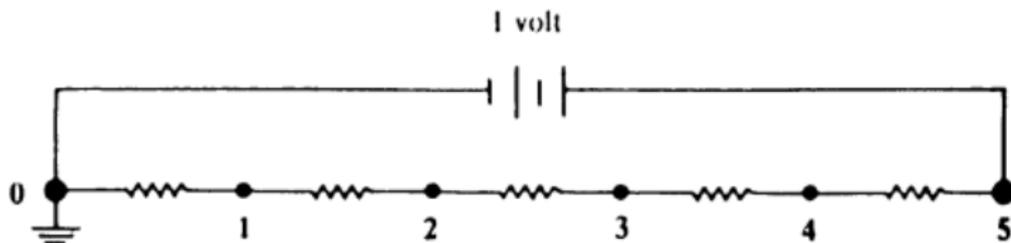

- Want to find voltage at each node  $v(x)$


# Similar Problem ?!

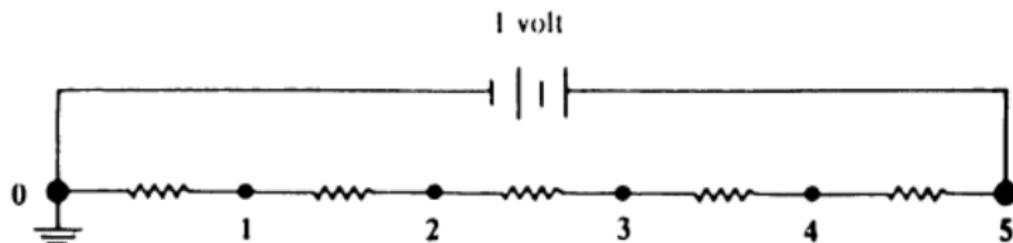

- Want to find voltage at each node  $v(x)$
- Ohm's Law & Kirchoff's Laws

$$v(x) = \frac{1}{2}v(x-1) + \frac{1}{2}v(x+1)$$

# Similar Problem ?!

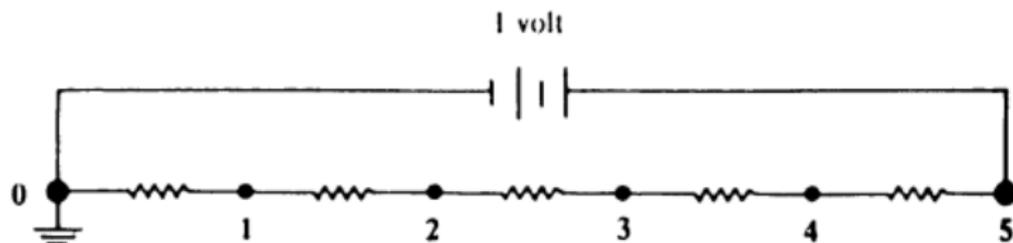


- Want to find voltage at each node  $v(x)$
- Ohm's Law & Kirchoff's Laws

$$v(x) = \frac{1}{2}v(x-1) + \frac{1}{2}v(x+1)$$

- Uniqueness theorem

# Similar Problem ?!

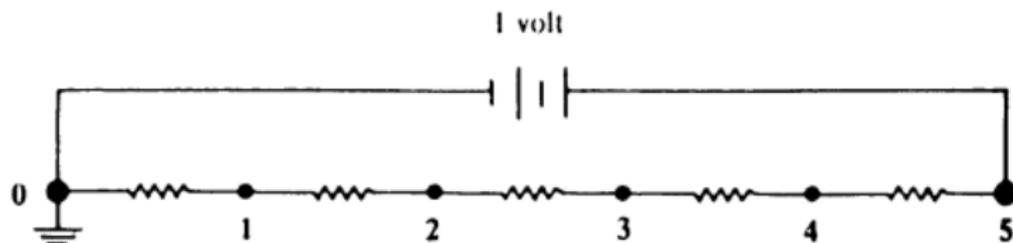


- Want to find voltage at each node  $v(x)$
- Ohm's Law & Kirchoff's Laws


$$v(x) = \frac{1}{2}v(x-1) + \frac{1}{2}v(x+1)$$

- Uniqueness theorem
- Escape probability is inverse of effective resistance

# More Dimensions

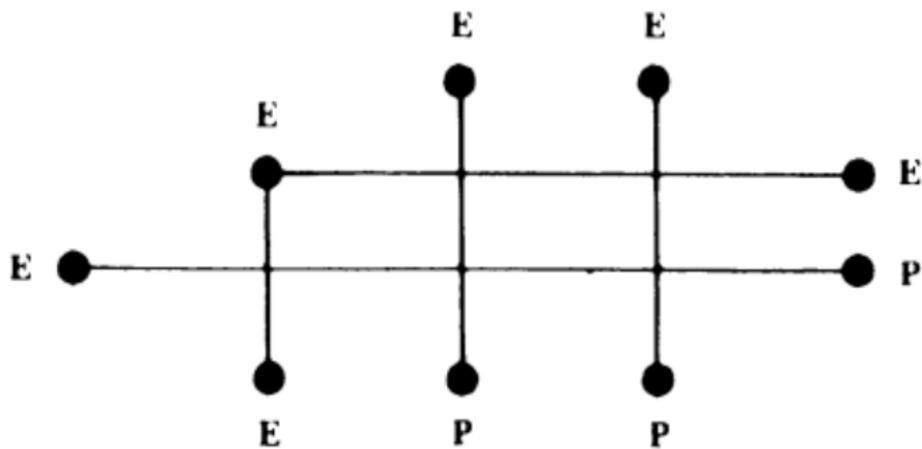

# More Dimensions

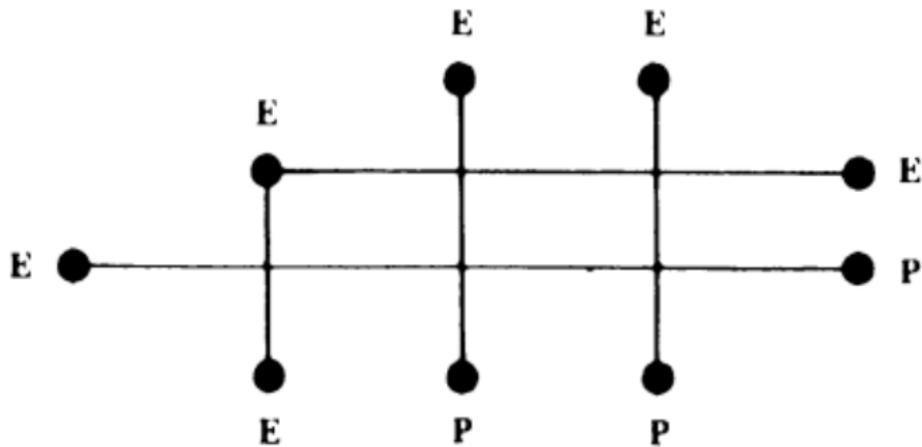


- E is escape, P is police
- What is the probability of escape before a policeman is encountered?

# More Recurrences


- Averaging principle from Law of Total Probability

$$f(a, b) = \frac{1}{4}f(a+1, b) + \frac{1}{4}f(a-1, b) + \frac{1}{4}f(a, b+1) + \frac{1}{4}f(a, b-1)$$

# Electric Analogue

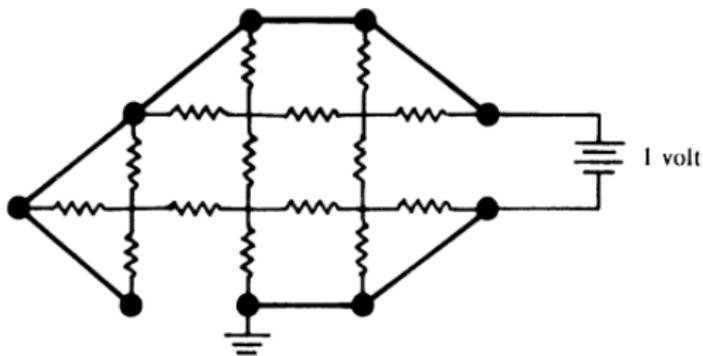

# Electric Analogue

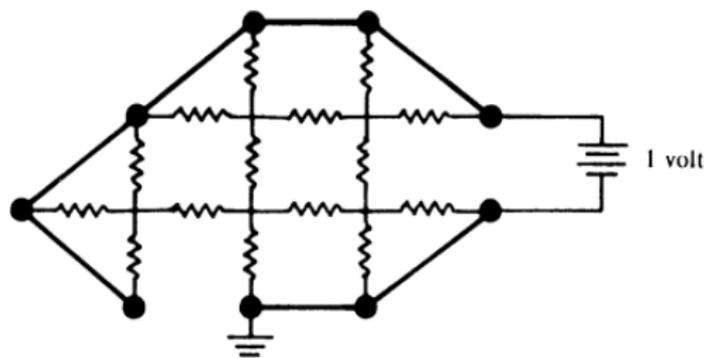


- Using Ohm's and Kirchoff's Laws, the voltage at each point  $v(a, b)$  is

$$v(a, b) = \frac{1}{4}v(a+1, b) + \frac{1}{4}v(a-1, b) + \frac{1}{4}v(a, b+1) + \frac{1}{4}v(a, b-1)$$


# Lattices and Infinite Random Walks



1-dimensional lattice

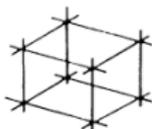

3-dimensional lattice

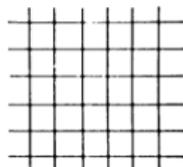


2-dimensional lattice


# Lattices and Infinite Random Walks



1-dimensional lattice

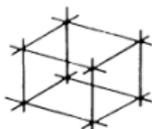

3-dimensional lattice

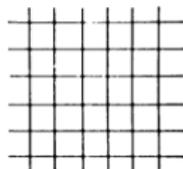


2-dimensional lattice

- $\mathbb{Z}^d$  is an infinite d-dimensional lattice


# Lattices and Infinite Random Walks



1-dimensional lattice

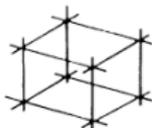

3-dimensional lattice

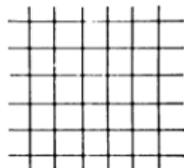


2-dimensional lattice

- $\mathbb{Z}^d$  is an infinite d-dimensional lattice
- Let  $\mathbf{0}$  be the origin or where the random walk started
- We want to find escape probability i.e. never returning to  $\mathbf{0}$
- **Recurrent** - escape probability is 0
- **Transient** - escape probability is nonzero


# Lattices and Infinite Random Walks



1-dimensional lattice

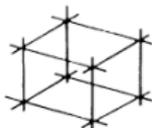

3-dimensional lattice

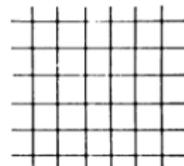

2-dimensional lattice

- $\mathbb{Z}^d$  is an infinite d-dimensional lattice
- Let  $\mathbf{0}$  be the origin or where the random walk started
- We want to find escape probability i.e. never returning to  $\mathbf{0}$
- **Recurrent** - escape probability is 0
- **Transient** - escape probability is nonzero
- **Type problem** - determining whether or not a random walk is transient or recurrent

# Electric Analogue (1D)



Resistance to infinity infinite!



# Electric Analogue (1D)



Resistance to infinity infinite!


- 1D is trivial

# Rayleigh's Monotonicity Law

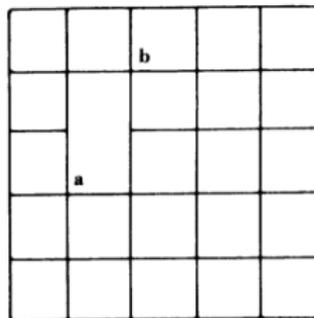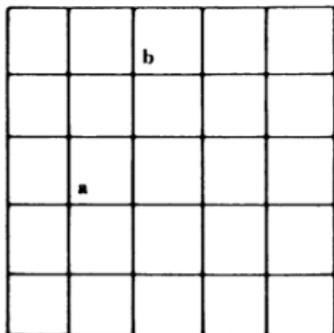


- Right is lower resistance than left

# 2D Random Walk

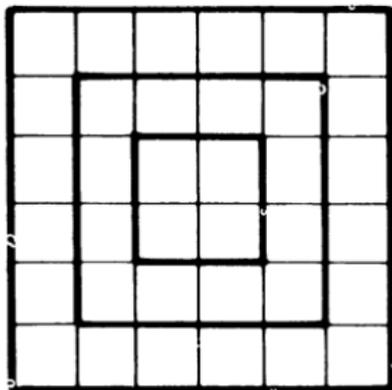


# 2D Random Walk

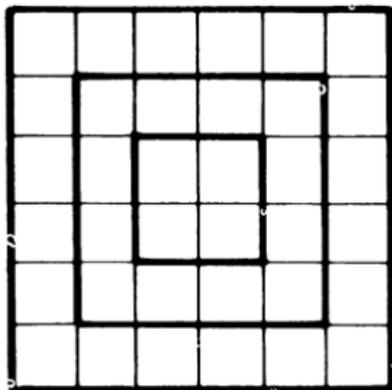

- Add up all the branches in parallel


## 2D Random Walk

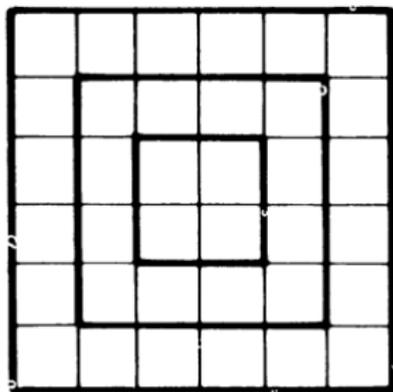


- Add up all the branches in parallel

$$\frac{1}{4} + \frac{1}{12} + \frac{1}{20} \cdots = \sum \frac{1}{8n+4} \sim \sum \frac{1}{n} = \infty$$

# Higher Dimensions

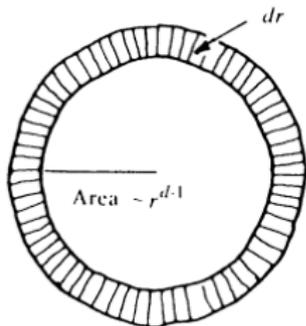

# Higher Dimensions

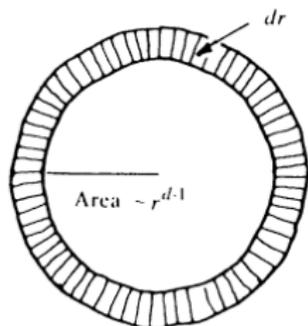

$$R_{\text{eff}} \sim \int_a^{\infty} \frac{dr}{r^{d-1}}$$

- Integral diverges only for  $d = 1, 2$

# Why This is Useful

# Why This is Useful

- Simplifies calculations greatly!

# References



## **Doyle et al.: Random walks and electric networks**

---



Peter G. Doyle and J. Laurie Snell. *Random walks and electric networks*. MAA Press, 2006. URL: <https://math.dartmouth.edu/~doyle/docs/walks/walks.pdf>.